

VLSI Design

Final Project Report


Name : T.Sri Vishnuvarun

Rollnumber: 2022102031


1)Verilog

Results from Verilog codes are shown below:


i)Full Adder:

 


ii) Four Bit Adder/Subtractor:

 


iii) Twotofour Decoder:

 


iv) AndBlock:

 

v) Comparator:

 


vi) Alu :

 

2)NG SPICE


The results from Ng spice simulations are shown below

i) Two to four decoder:

 


The below are the results from main Alucircuit when each operation is done separately


ii) Adder Block:

 


iii)Subtractor

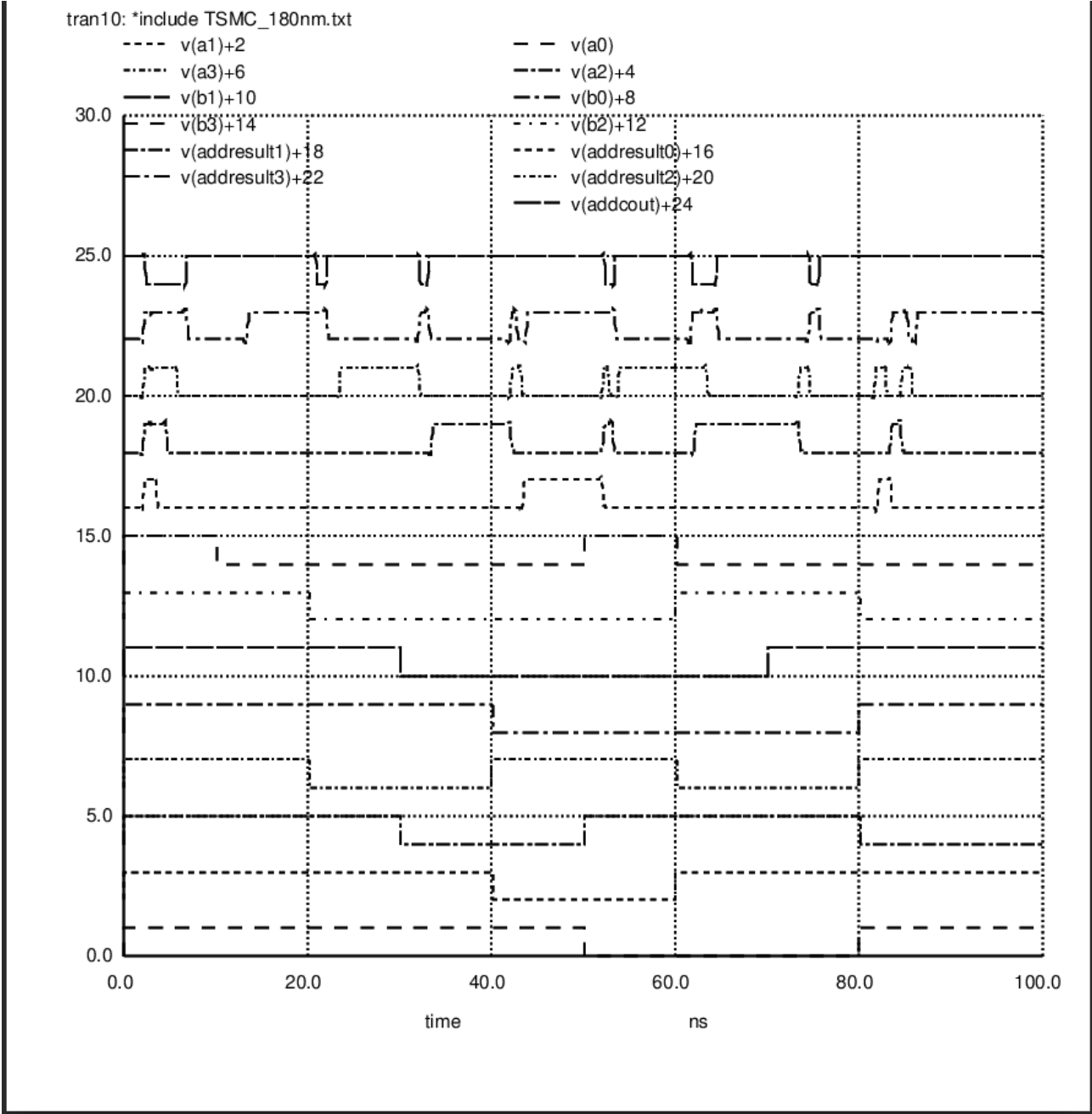

iii)Comparator:

 

iv)Andblock:

 

3) MAGIC